

The MOS Differential Pair

Aditya Sudhakar
Manu Patil
Shashank Swaminathan

April 8, 2020

All experiments were conducted in LTspice.

Experiment 1: Differential Pair Current-Voltage Characteristics

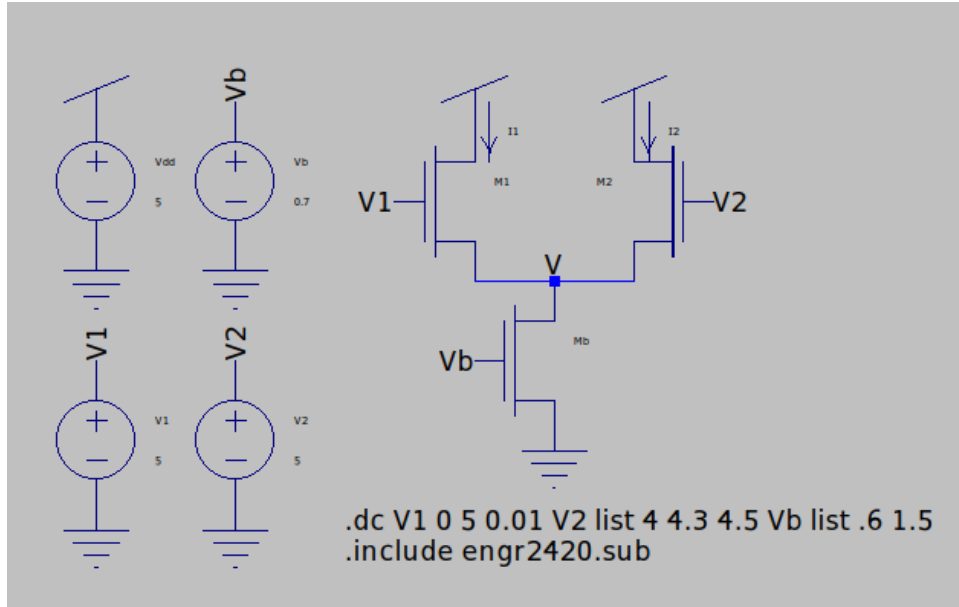


Figure 1: Schematic for Experiment 1

In Weak and Moderate Inversion

As seen on Figure 2, the current-voltage characteristics are almost identical for changing values of V_2 . There is no significant change in these characteristics as V_2 changes.

As seen in Figure 3, the voltage seen on the common source node of the bias transistor is constant for values when V_1 is less than V_2 , expressed as values under 0V on our plot. At $V_2 - V_1 = 0V$ there is an slope on the graph and the voltage measured on the common source node of the bias transistor climbs linearly as V_1 becomes greater than V_2 .

The transconductance gain G_{dm} does not change significantly with changes in V_2 . In the weak inversion case, the change has a magnitude on the order of 10^{-8} , which is insignificant.

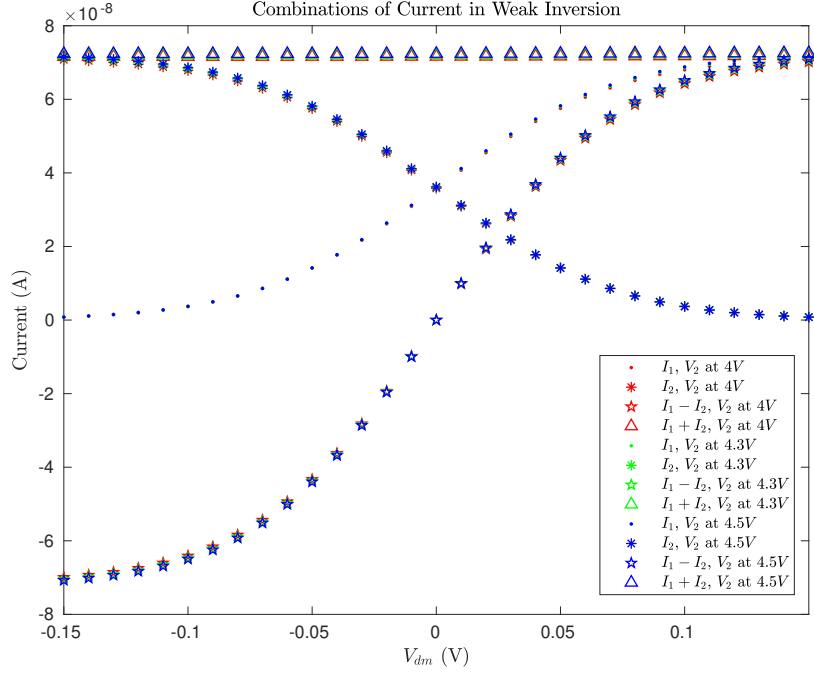


Figure 2: $I_1, I_2, I_1 - I_2$, and $I_1 + I_2$ as a function of $V_1 - V_2$ for V_2 @ 4V, 4.3V, 4.5V

V_2	WI
4V	$968.8n\Omega$
4.3V	$978.1n\Omega$
4.5V	$984.2n\Omega$

Table 1: Extracted G_{dm} values for Weak Inversion modes for different V_2 values

In Strong Inversion

As seen on Figure 4, the current-voltage characteristics are almost identical for changing values of V_2 . There is no significant change in these characteristics as V_2 changes.

As seen in Figure 5, the voltage seen on the common source node of the bias transistor is constant for values when $V_1 - V_2$ is less than -0.75V on our plot. At $V_2 - V_1 = 0.75V$ there is a change in slope on the graph and the voltage measured on the common source node of the bias transistor climbs linearly as V_1 becomes greater than V_2 .

The transconductance gain G_{dm} does not change significantly with changes in V_2 . In strong inversion, the change has a magnitude of 10^{-7} , which is insignificant compared to the change in V_2 .

V_2	SI
4V	$44.97\mu\Omega$
4.3V	$44.90\mu\Omega$
4.5V	$44.84\mu\Omega$

Table 2: Extracted G_{dm} values for Strong Inversion region for different V_2 values

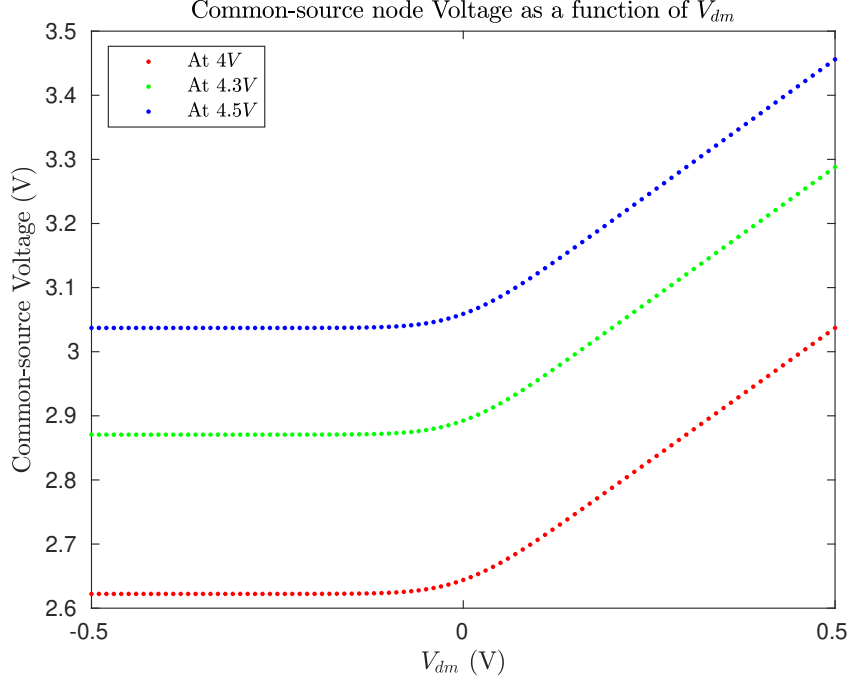


Figure 3: Voltage at the source of the bias transistor as a function of $V_1 - V_2$

Comparing the Response to Different Levels of Inversion

G_{dm} is much larger in strong inversion than in the weak and moderate inversion levels. This means that the circuit takes more time to become a source follower for either transistor. It's evidenced in the graph of the response - the circuit takes $\pm 1V$ from $V_{dm} = 0$ to settle into a source follower case for strong inversion, compared to $\pm 0.2V$ in the weak and moderate inversion cases. Additionally, the range of current spanned by the circuit's response in the strong inversion case is about 3 orders of magnitude greater than that of the circuit's response in the weak and moderate inversion cases.

Finally, the common-source node voltage V is also affected by the inversion case. It has larger values for the same values of V_2 in weak and moderate inversion than it does in strong inversion. It switches from a constant value to a steadily increasing value at an earlier point ($V_{dm} \approx -0.75V$) in strong inversion than in weak and moderate inversion ($V_{dm} \approx 0V$). The increasing behavior of V past this switch point looks more linear in the weak and moderate inversion cases than in the strong inversion case.

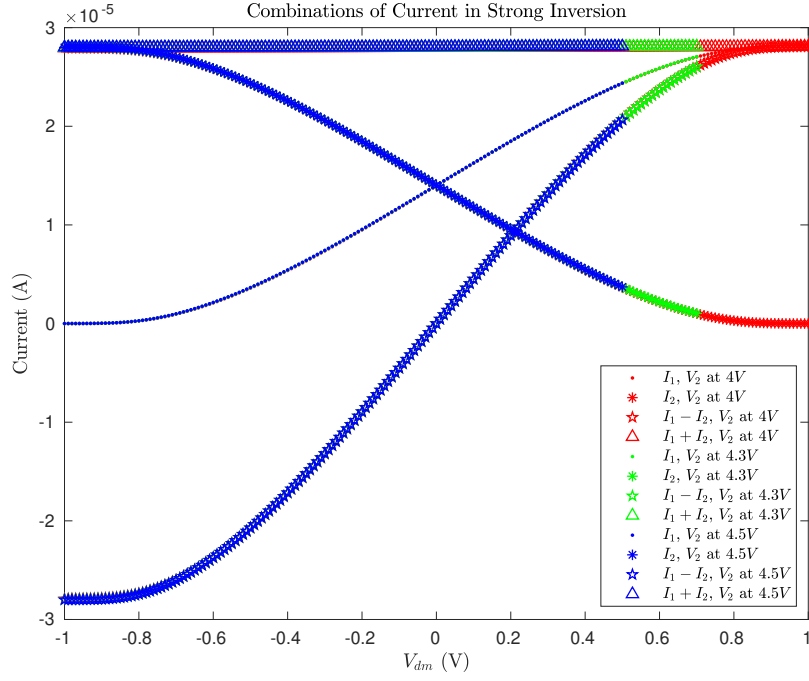


Figure 4: $I_1, I_2, I_1 - I_2$, and $I_1 + I_2$ as a function of $V_1 - V_2$ for V_2 @ 4V, 4.3V, 4.5

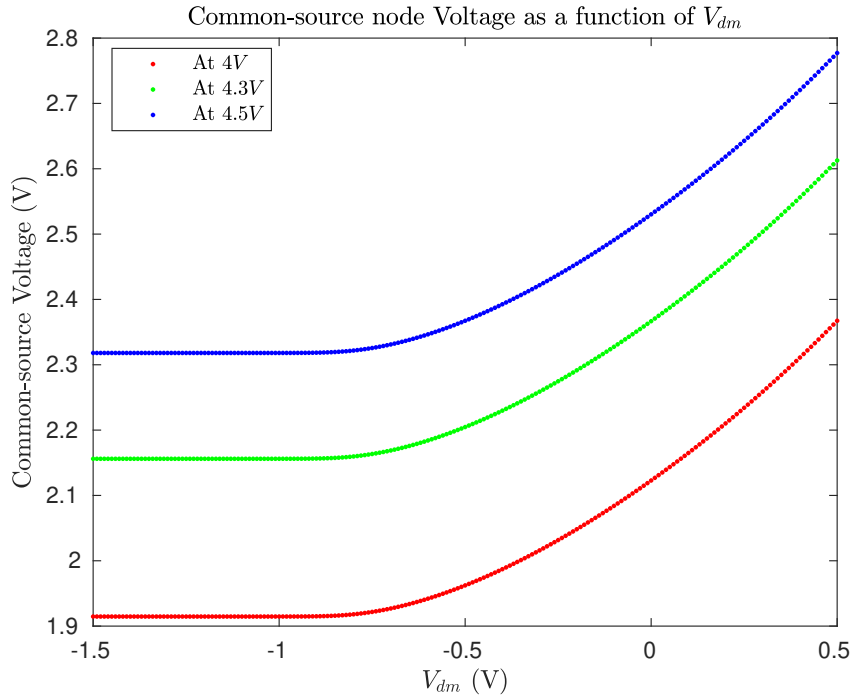


Figure 5: Voltage at the source of the bias transistor as a function of $V_1 - V_2$